

# LECTURE 10

AC Circuits  
and  
Sampling Labs

# Schedule Change

- AC Circuits will be Monday and Tuesday
- Sampling Lab will be Wednesday and Thursday

# Outline— AC Circuits

- Safety for circuits with  $>50$  volts
- Prelab material
- Lab tests
- Results


# Basic electrical safety

- Electrical injuries due to tissue heating, nerve system disruption, reflex actions, arc burns.
- 5 ma is the “let go” current
- Path of current through the body is important
- Body impedance is primarily in the skin



# Laboratory Safety Procedures

- Eye safety– goggles
- Work only on dead circuits
- Have instructor check circuit before energizing
- Avoid having to reach across hot resistors/hot wires
- No loose jewelry
- Work with one hand


# Theory

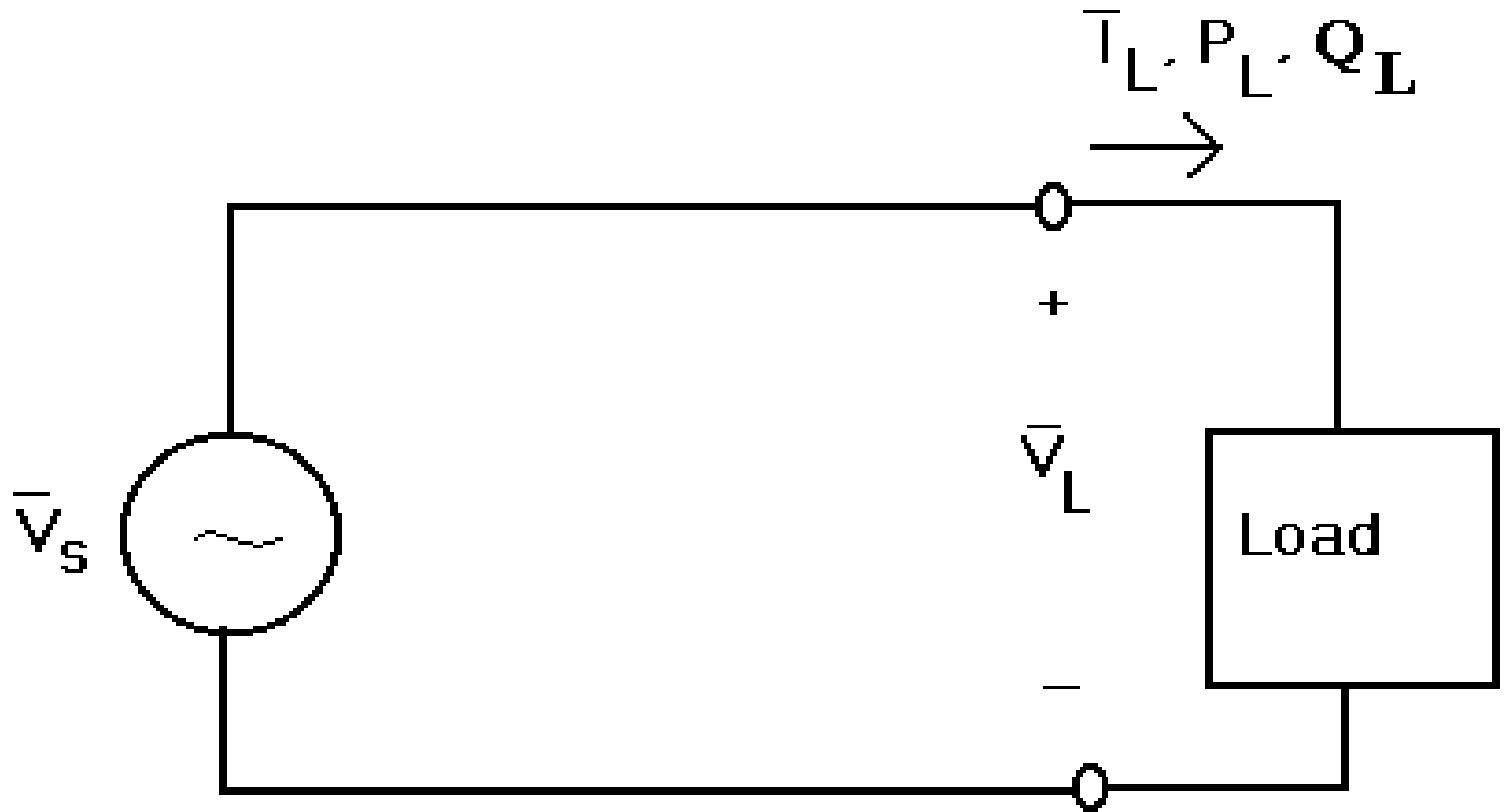

# RL Load

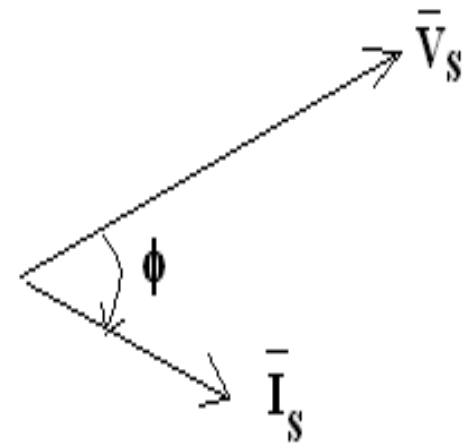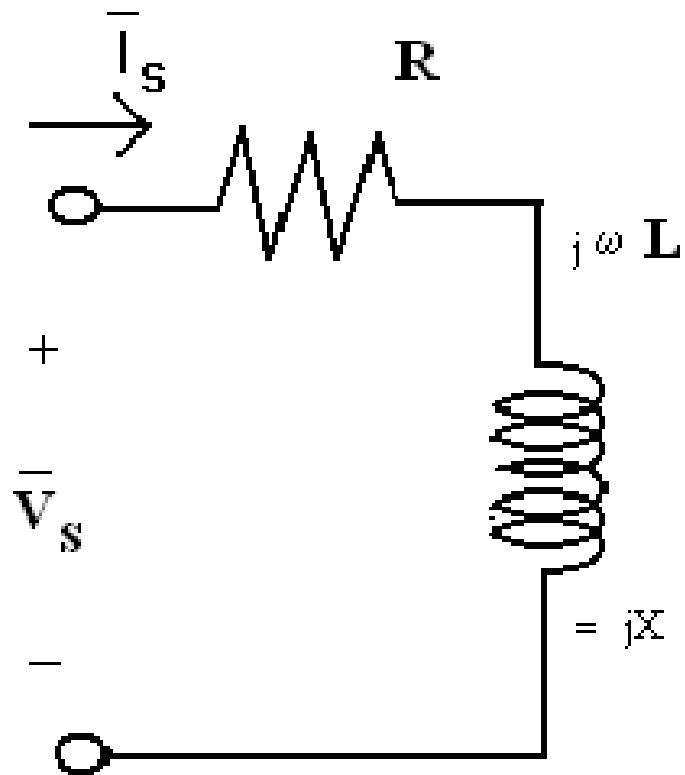

# Power Triangle

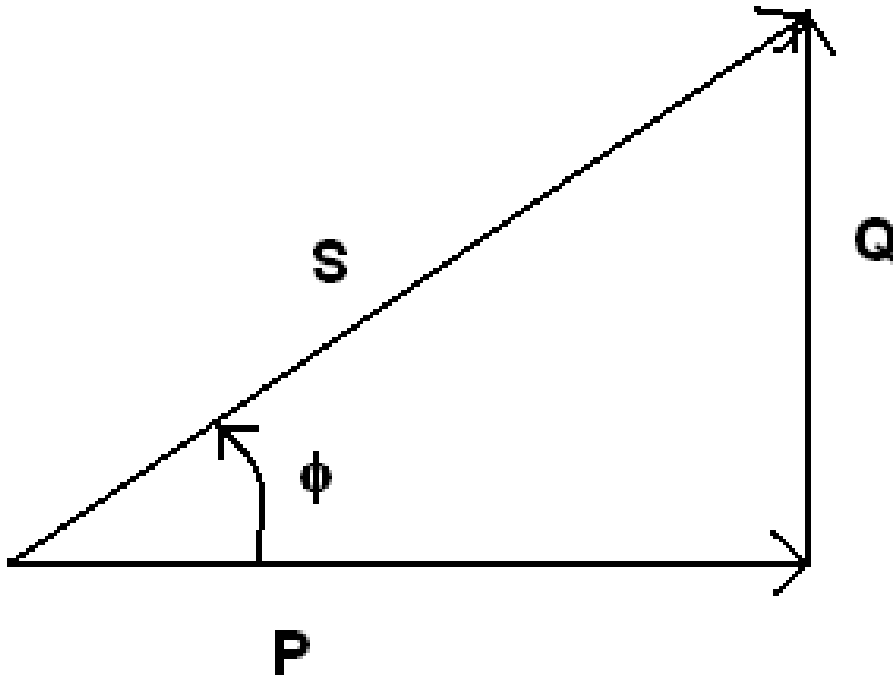

$$S=VI= \text{volt-amps}$$

$$P=VI\cos\phi= \text{watts}$$



$$Q=VI\sin\phi= \text{vars}$$

$$\text{power factor}=\frac{P}{S}$$

$$=\cos(\phi)$$

$$S^2=P^2+Q^2$$



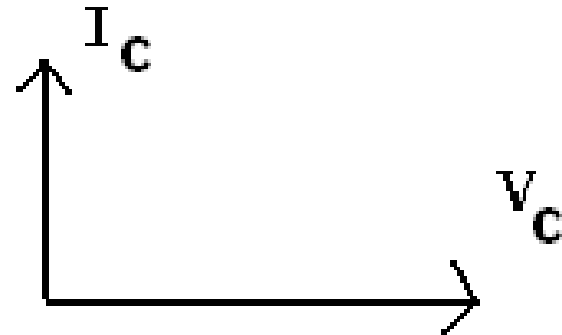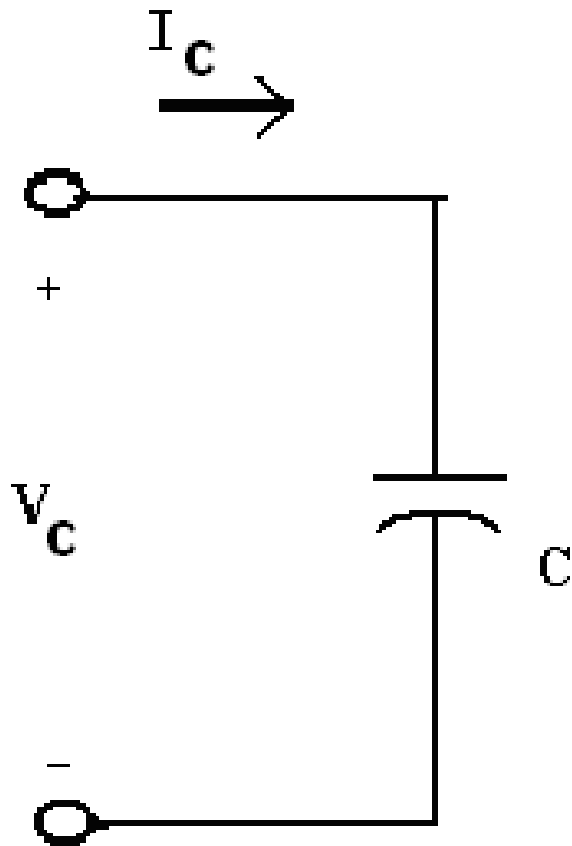

$$P_{\text{cap}} = 0$$


$$Q_{\text{cap}} = -V_c I_c$$

**NEGATIVE** vars flow **TO** the cap

**POSITIVE** vars flow **FROM** the cap

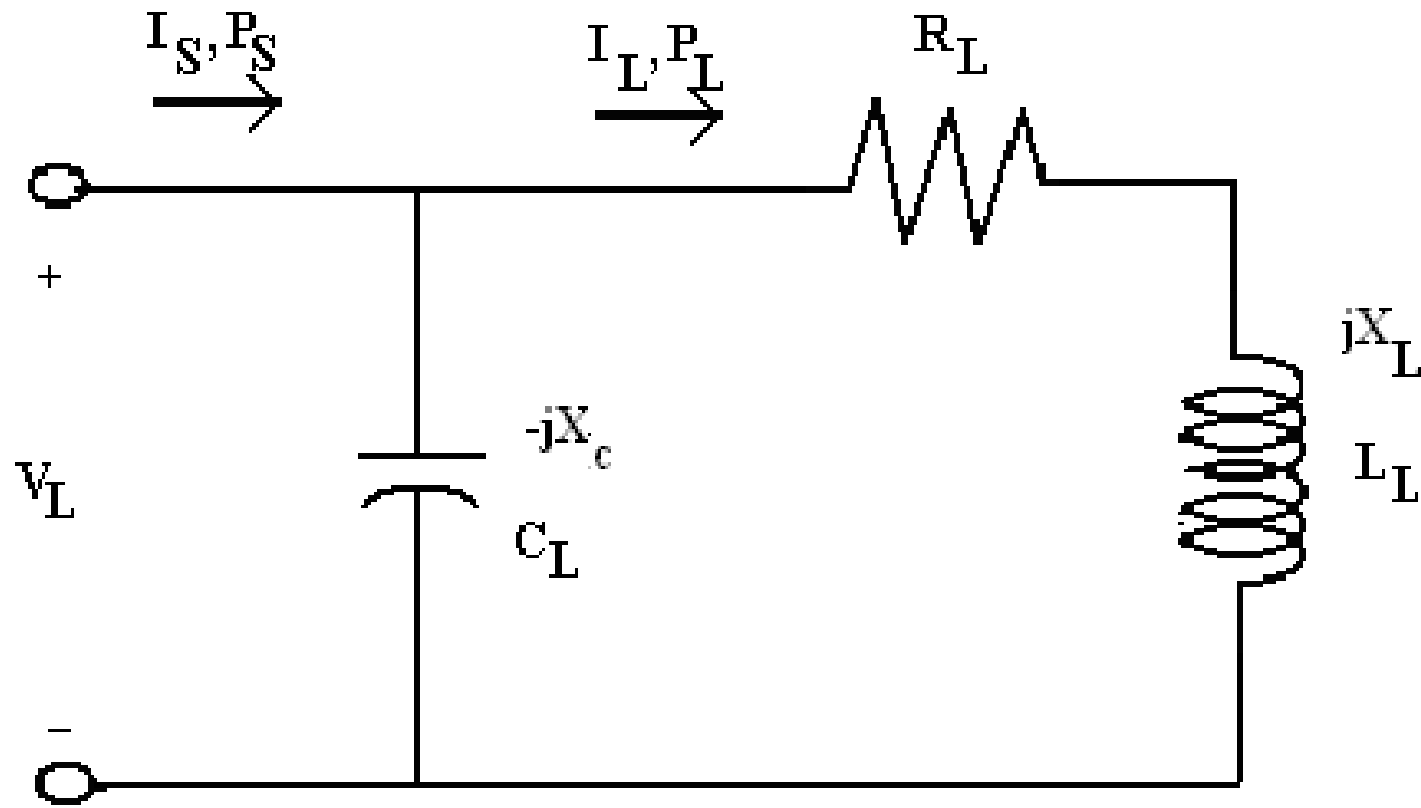
# Measurements

- Measure  $V$  (volts),  $I$  (amps), and  $P$  (watts)
- $S=VI$
- $\phi = \cos^{-1}(P/S)$
- $Q = (S^2 - P^2)^{1/2}$



Constant  $V_L$  means constant  $I_L$  and  $P_L$  as  $C_L$  changes

# Measurement circuit

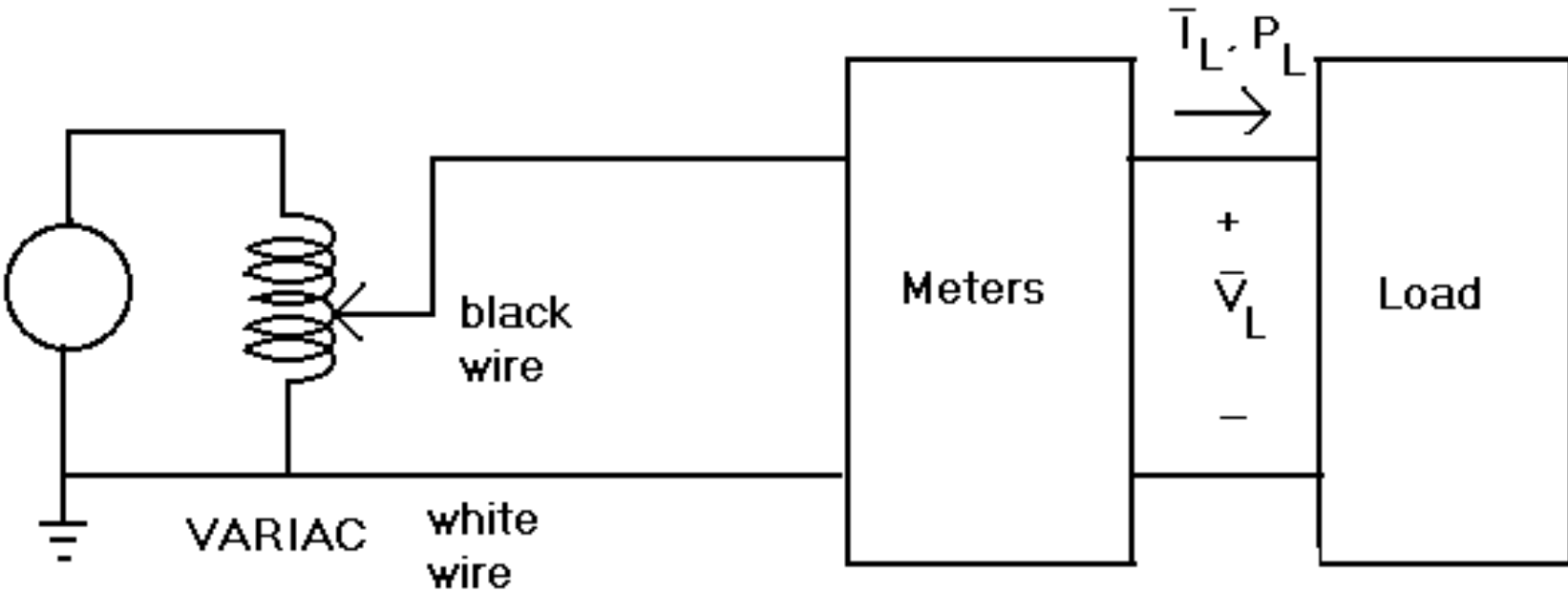

# Metering circuit

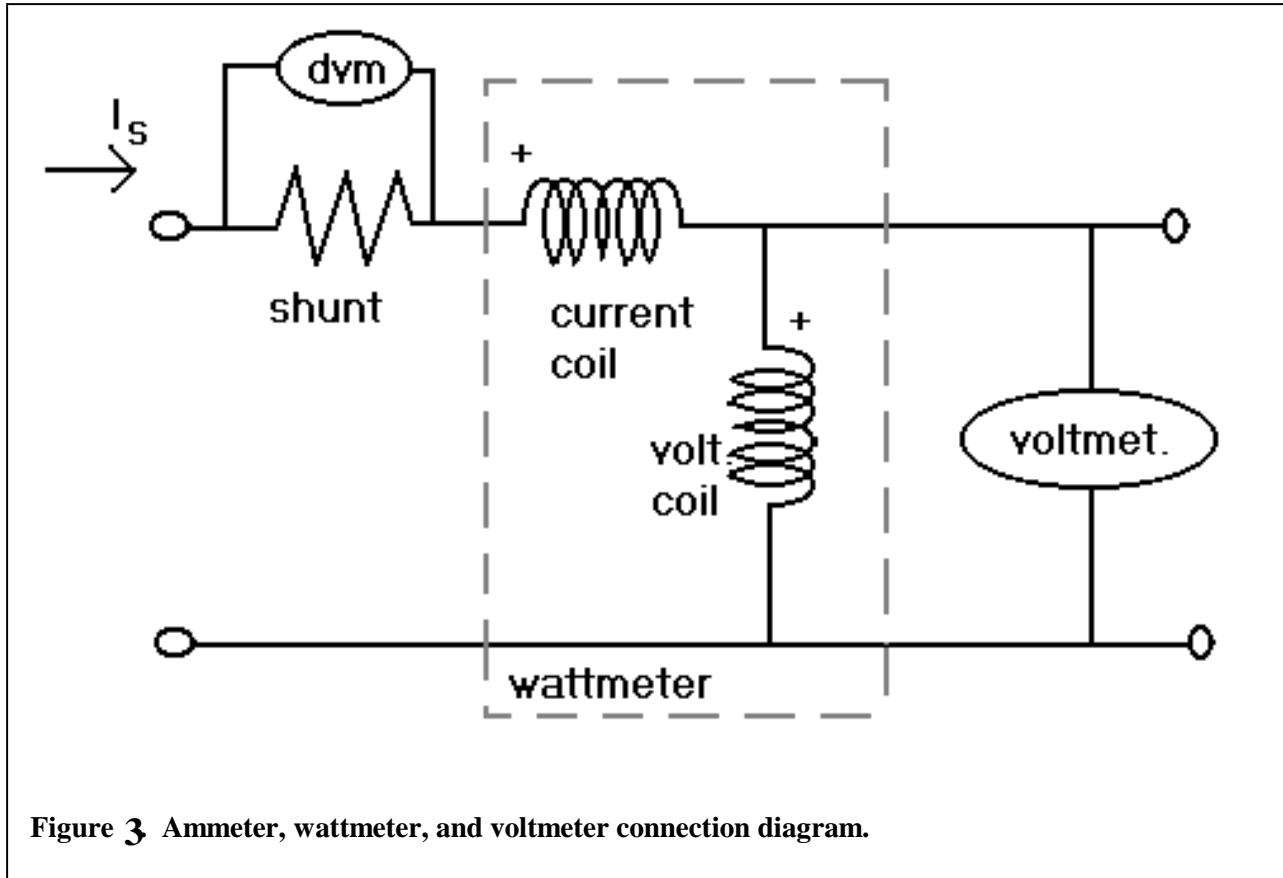


Figure 3 Ammeter, wattmeter, and voltmeter connection diagram.

# Results

- C will generate vars—L will consume vars
- If capacitive vars = inductive vars, there will be unity power factor (and minimum source current)
- Further increase in capacitance will create a leading power factor (and current will be larger)

# Results


- For each operating point—
  - Measure  $V$ ,  $I$  and  $P$
  - Calculate  $S$  and  $\phi$
  - Draw power triangle to scale
  - Determine capacitive vars from the source measurement
  - Predict capacitive vars by formula  $\omega CV^2$

# Sampling Lab-- Objectives


- Use shift registers in LabView
- Use continuous sampling to estimate signal characteristics
- Integrate and differentiate signals in real time


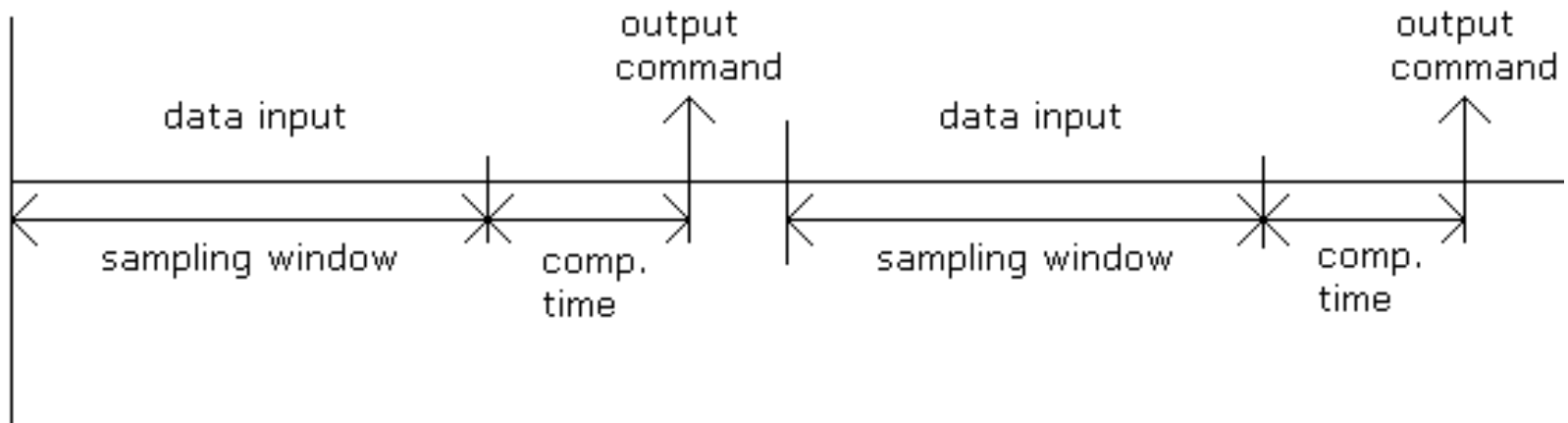
# Windowed Data Gathering (what we did previously)




# Continuously sampled signal

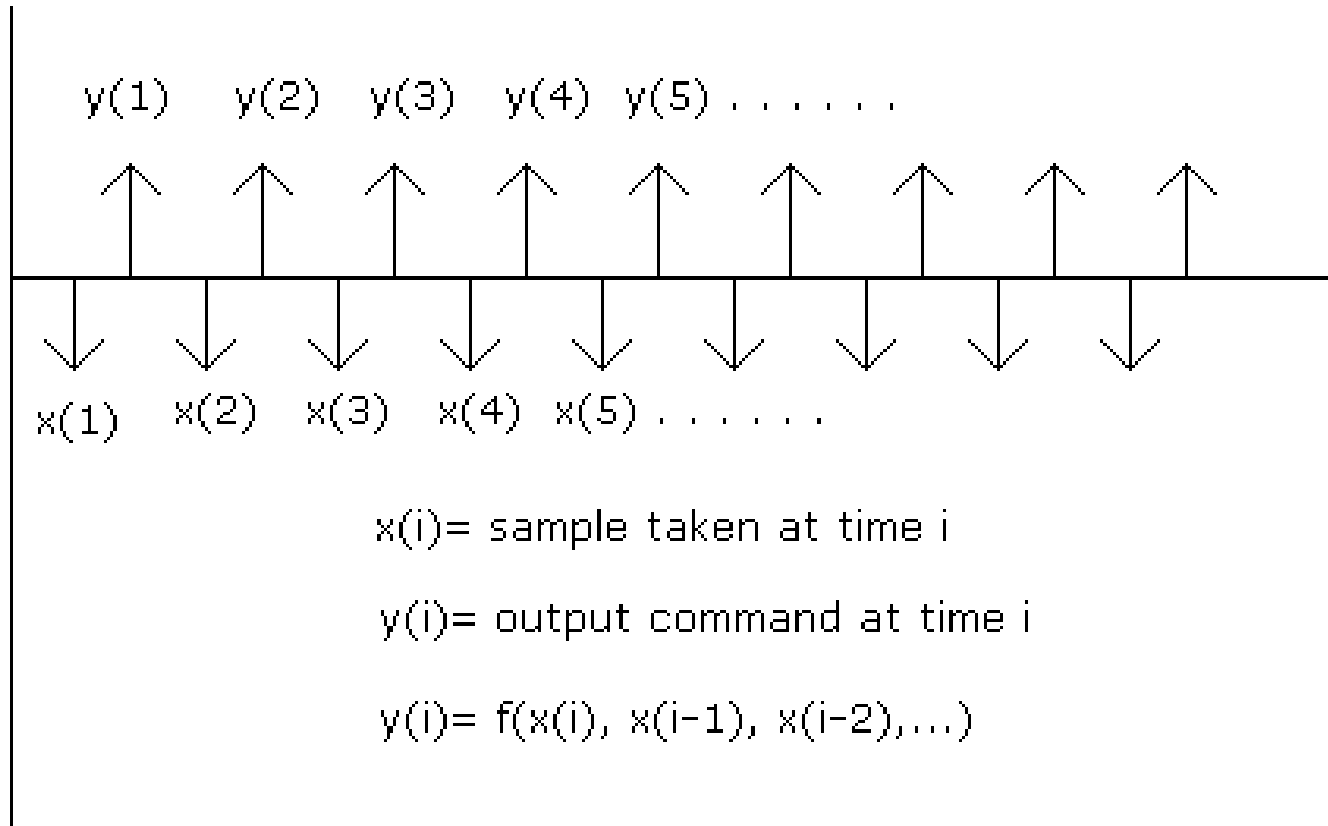


# Comparison

- Suppose the sampling theorem dictates a sampling rate of 1khz.
- Suppose you need to have 100 samples to characterize the wave
- In windowed data, you could make a decision no quicker than every 0.1 sec.
- In continuously sampled data, you can make a decision every 1 millisecond.


# Shift Registers

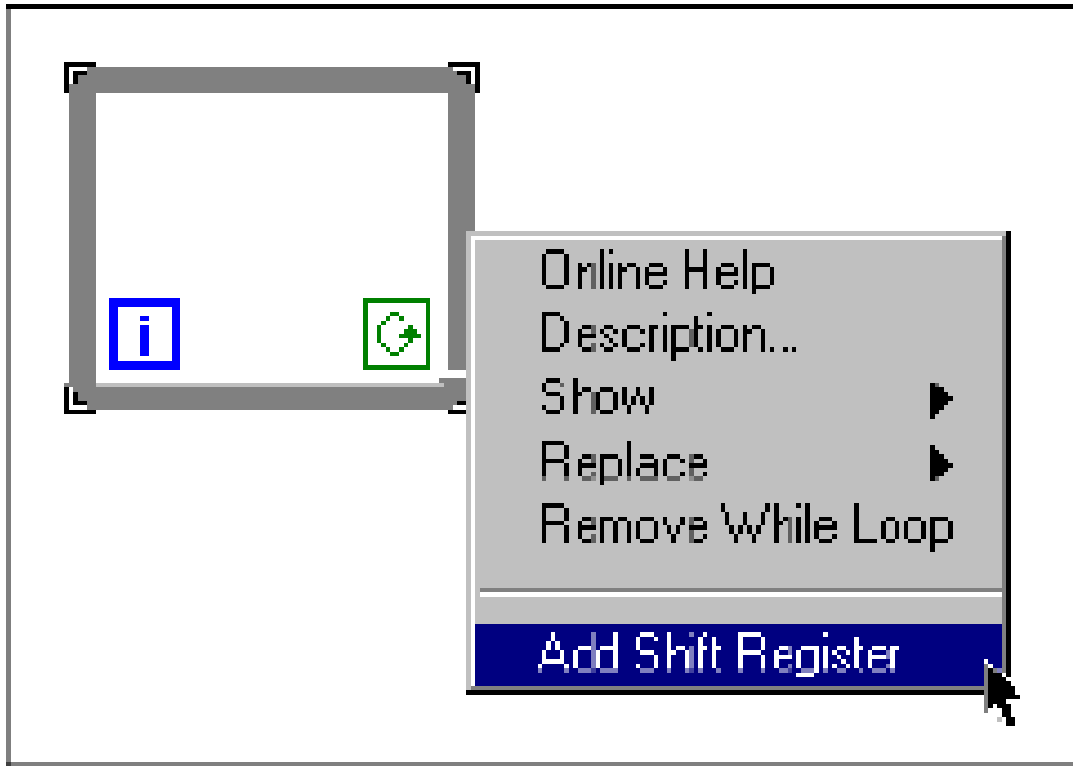


Before Loop Begins

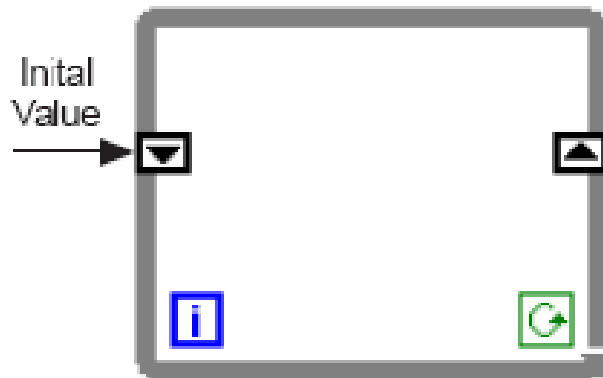


First Iteration

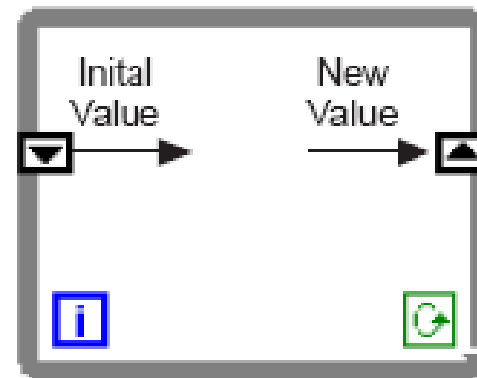


Subsequent Iterations

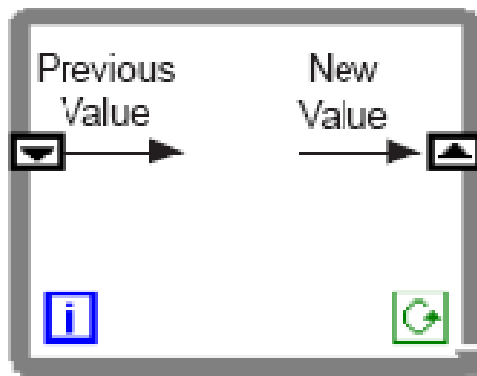


Last Iteration

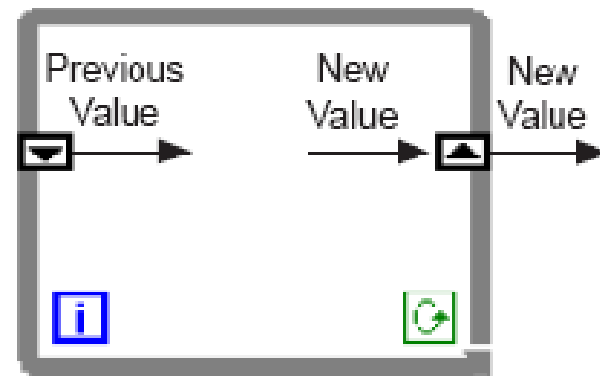

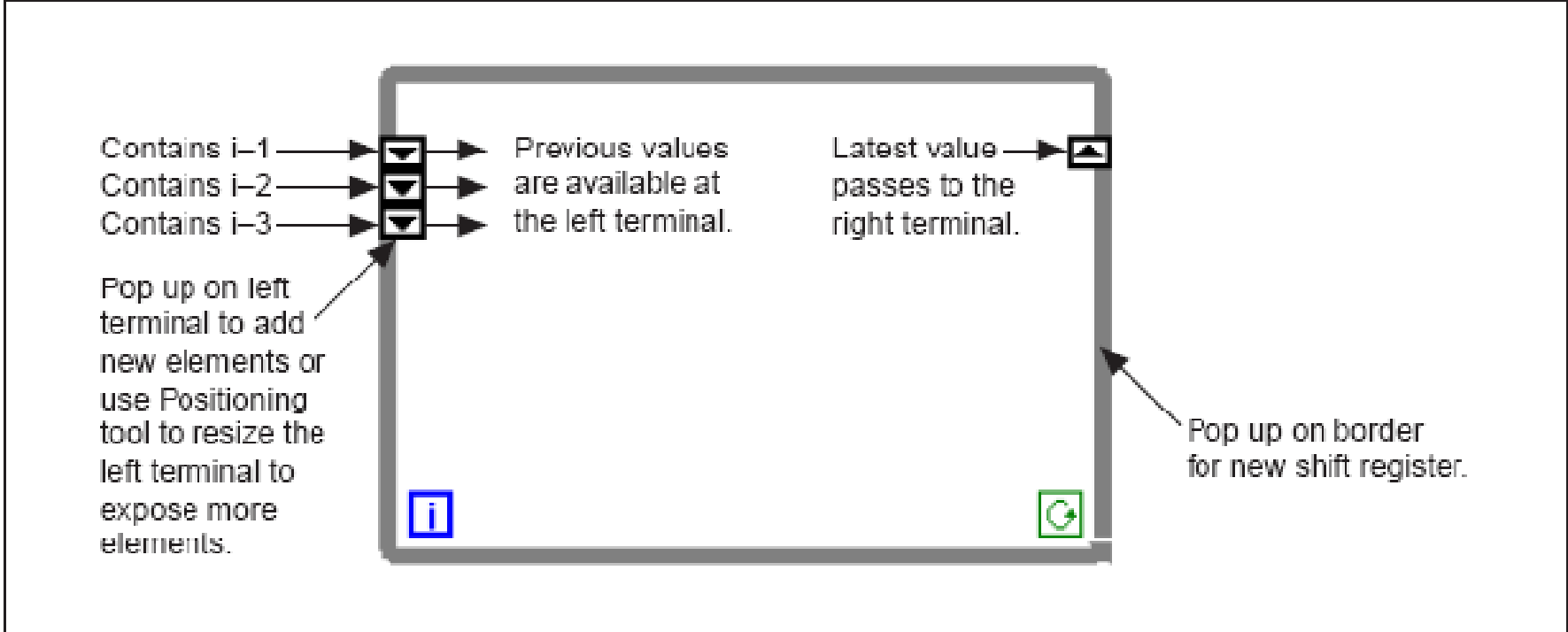

# Averaging Circuit

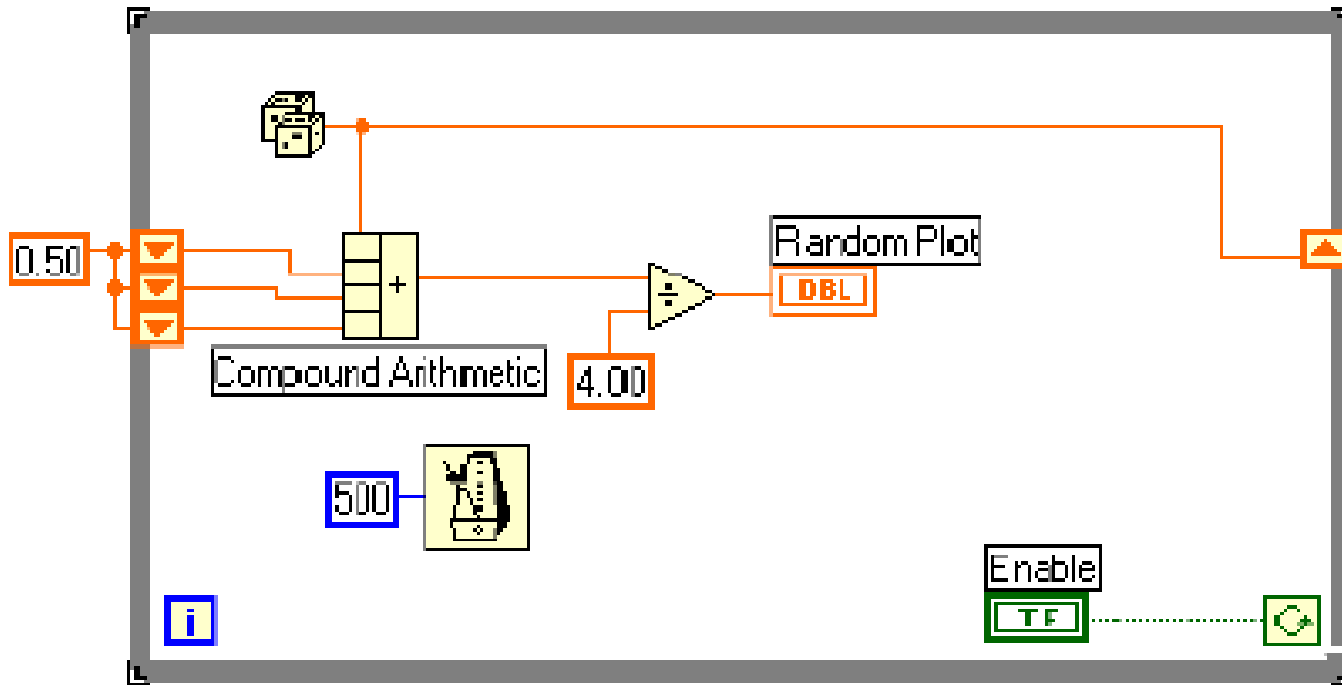


# We will do...


- Averaging
- Integrating
- Differentiating
- RMS'ing



# Real Time Integration-- discretization

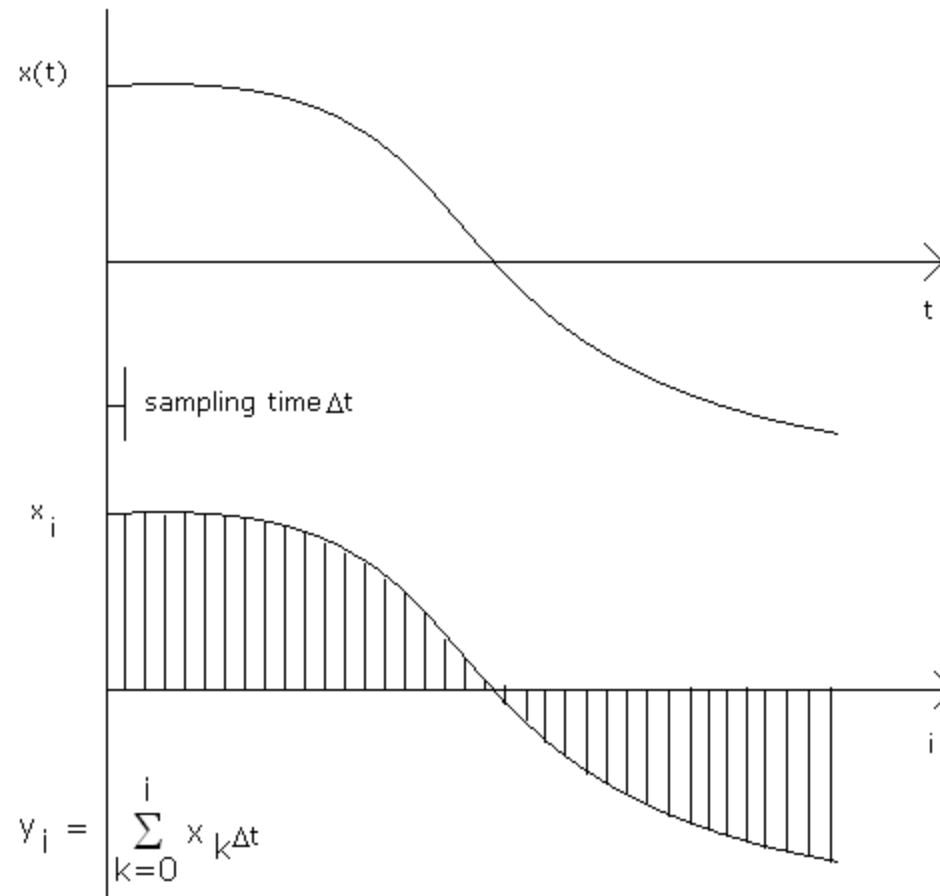

# Integration-- summation

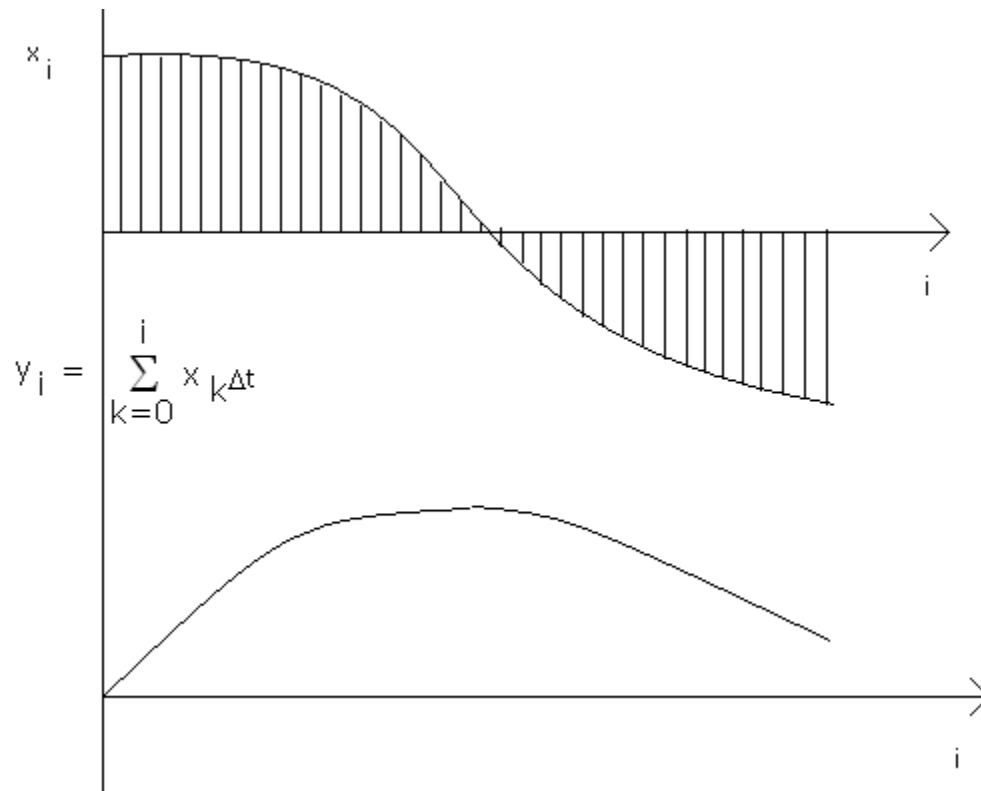

# Algorithm

$$y(i) = \sum_{k=0}^i x(k) \Delta t = y(i-1) + x(i) \Delta t$$

# What is the integral of a...

- Sine wave?
- Square wave?
- What is the derivative of these signals?
- How would you do a running RMS?