

EE 211

Lecture 6

Feb. 24, 2006

Topics

- Mid term exam
- Prelab policy
- Pspice Analysis
- Frequency Response

Mid-term Exam

- Closed book, closed notes
- 1 hour, in class
- Bring calculators
- Covers Labs 1-12
- Expect at least one question from each lab
- Short answer format similar to the example— expect 25 questions.

Prelab policy

- We will now begin collecting and grading all prelab materials.

Labs 12-13 Pspice Analysis

- Pspice is a circuit simulator program
- It uses libraries of components to define circuits and simulate them.
- Probe provides graphical output for the results
- Pspice includes transient, dc, transfer function, and other simulations modes

Pspice circuit files

Passive components– R, L and C

The 1st character in a name defines the device type.

The name is followed by the node numbers. The final number is the value of the component.

```
CANG2 610 605 1.0ufd
```

```
RANG2 605 0 10kohm
```

```
*
```

```
*field circuit
```

```
RF 630 632 0.001 ; field resistance
```

```
LPF 633 634 .2546mH
```

```
VF 630 0 .002
```

Independent Sources

V=voltage source

I= current source

Examples of DC, sinusoidal, and pulse voltages.

VF 630 0 .002volts

* (offset mag freq td df angle)

VBUSA 200 0 SIN(0 1.414V 60.0 0 0 0)

* initialval finalval delay risetime falltime pulse width period

IPMECH 0 600 pulse (1.0A 0.0A 0 0.01msec 0.01msec 40msec 100msec)

The Main circuit for a comparator

- The main Program

```
vi 11 0 sin(0 2 100 0 0)
```

```
* op-amp terminals: +in -in +ps -ps out
```

```
xOAmp          11  0  14  15  20  LM741/NS
```

```
Vcc 14 0 dc +12v
```


```
Vee 15 0 dc -12v
```

```
Rout 20 0 1kohm
```


- NOTE----- X indicates a call to a subcircuit

Transient Analysis

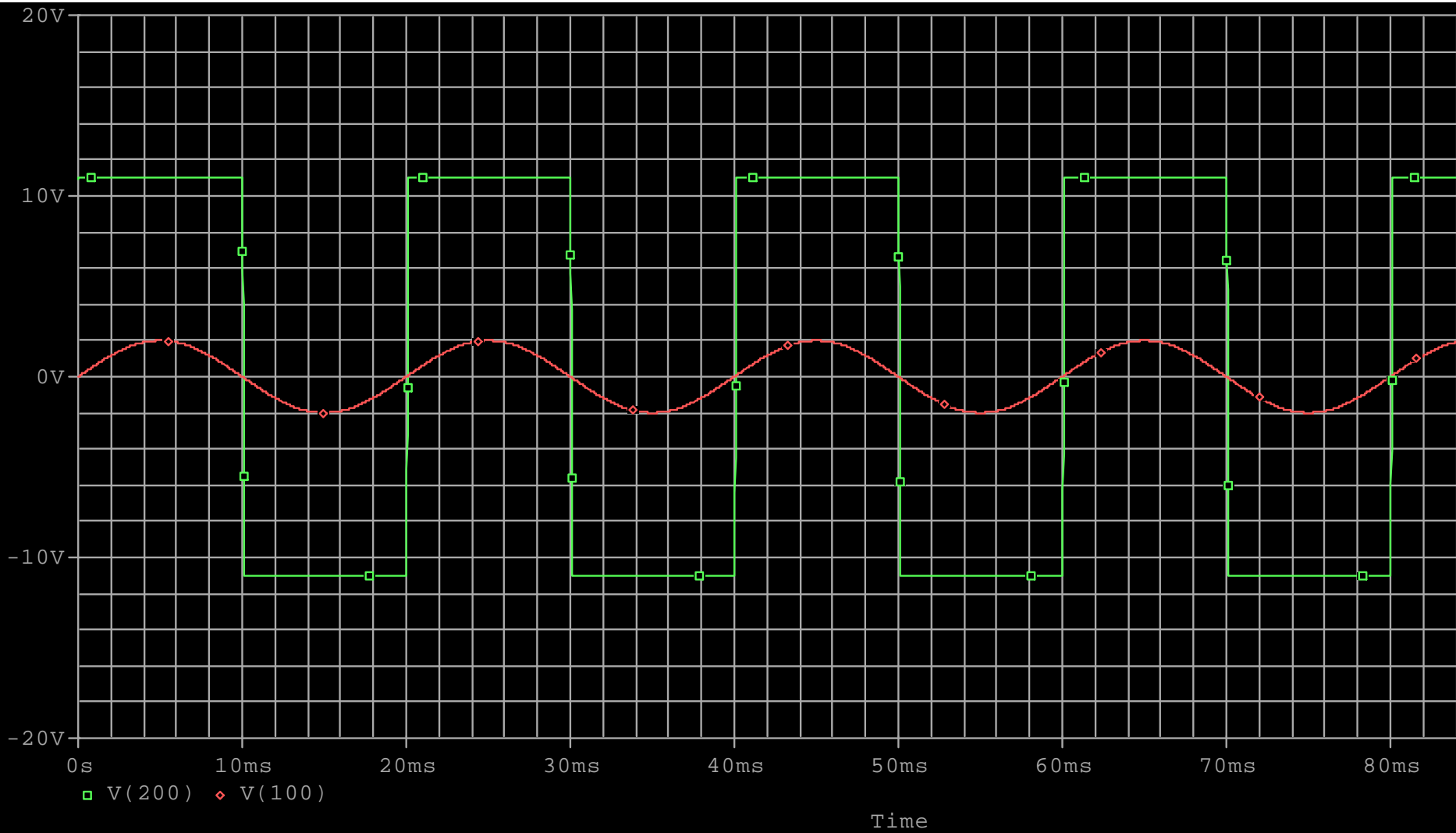
```
*      max step      Tend      print delay      max print step size
.tran 0.01ms        50ms        0ms              0.01ms
.probe
.end
```




Frequency Response- Gain vs. freq.

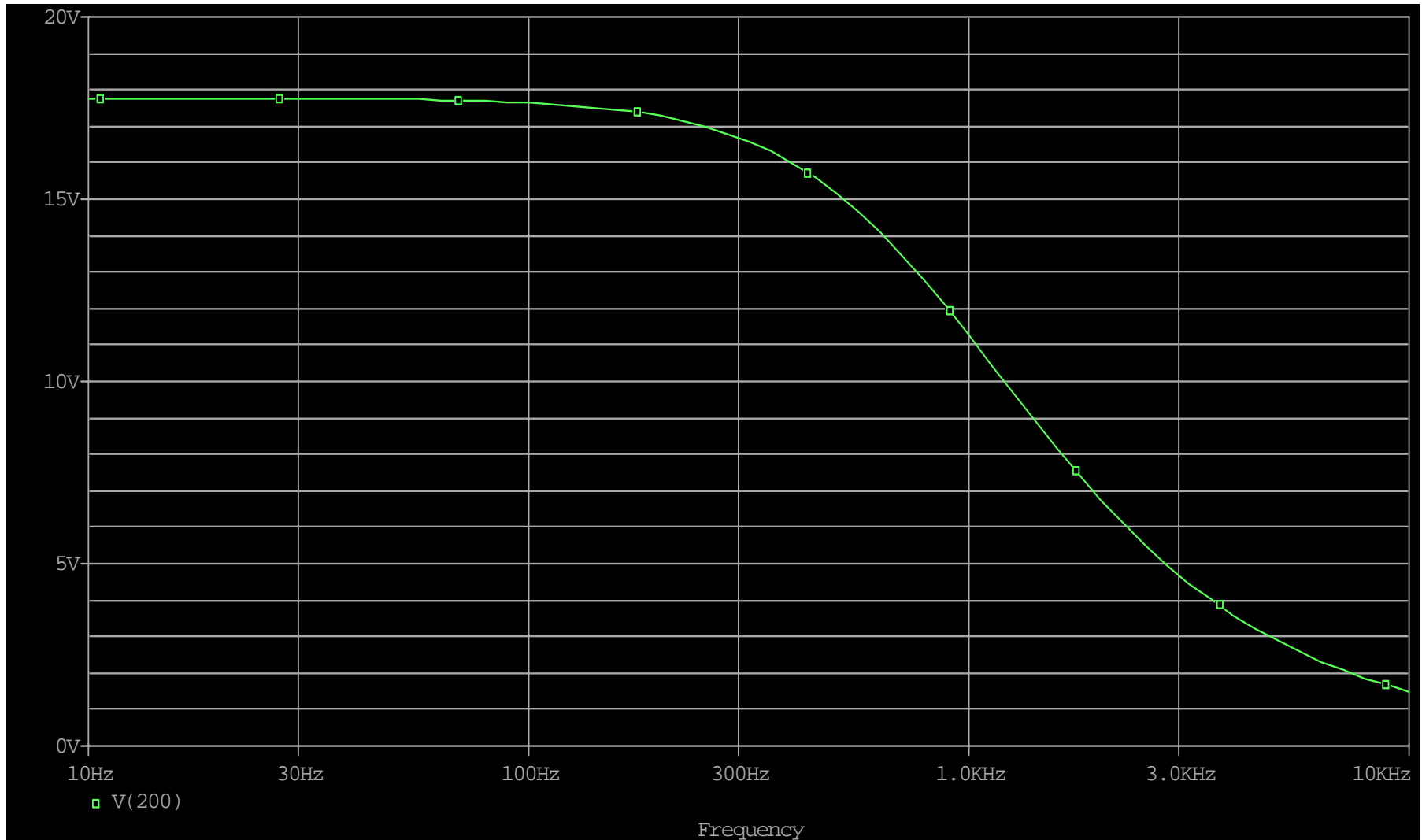

Frequency Response- Gain in db

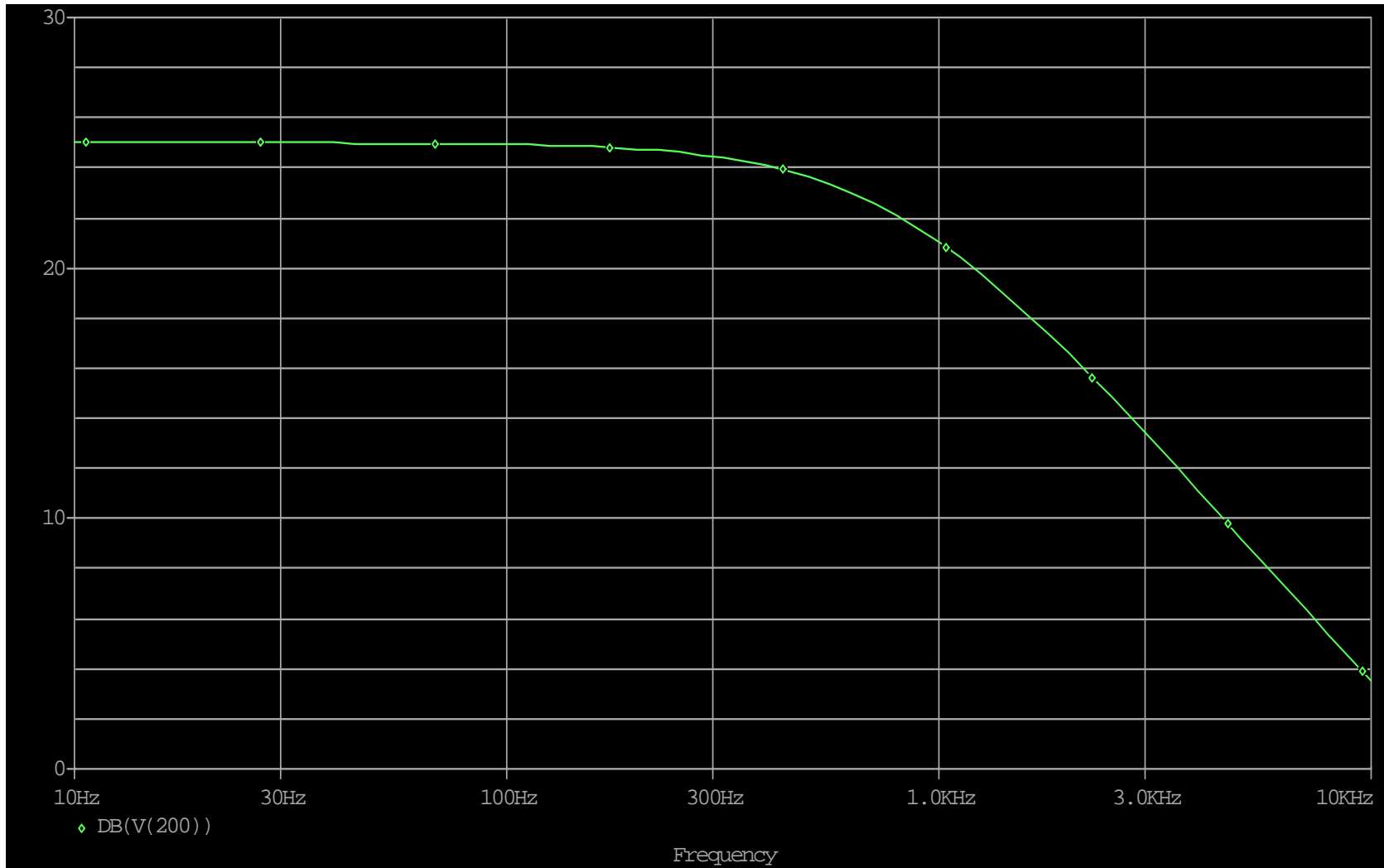

Low pass filter

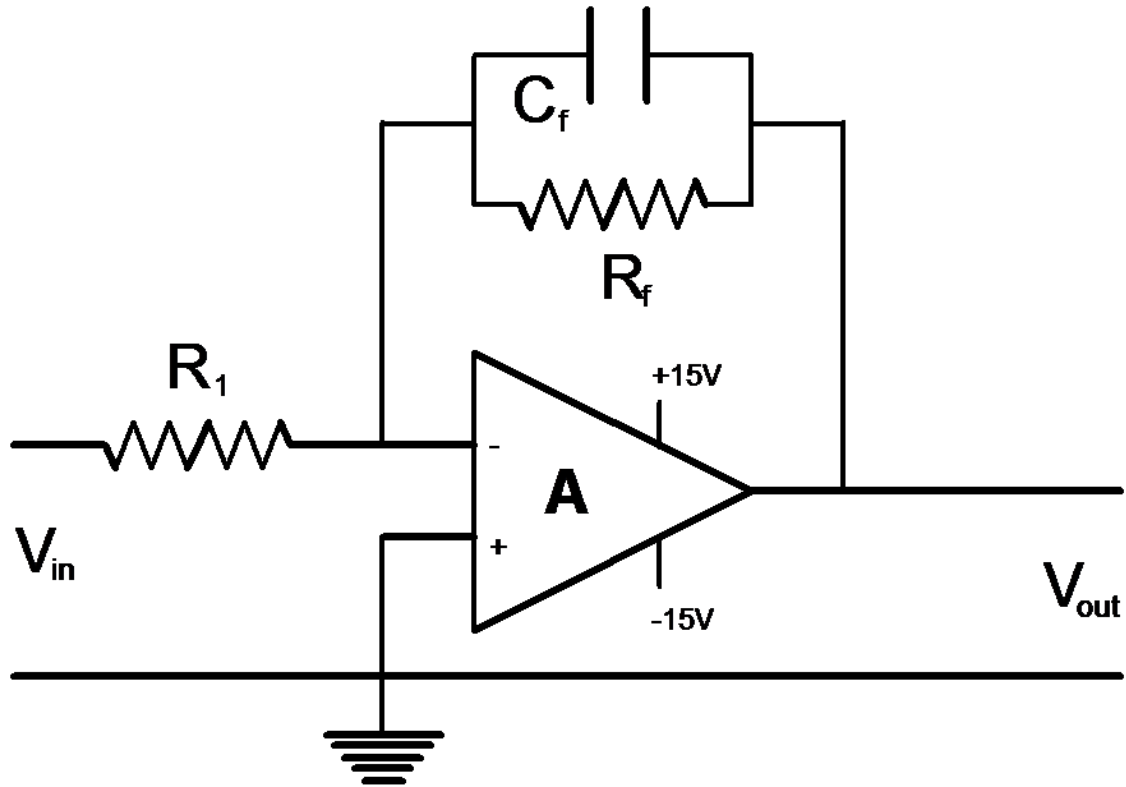

The feedback circuit impedance

A parallel RC circuit has an impedance of

$$Z_p(s) = \frac{1}{\frac{1}{R_p} + sC_p} = \frac{K_p}{1 + \frac{s}{\omega_p}}$$

Summary

- We will use Pspice, Labview and the lab bench to investigate low, high and bandpass filters.