

# VLSI Design

## CMOS Transistor Theory





# Outline

---

- Introduction
- MOS Capacitor
- nMOS I-V Characteristics
- pMOS I-V Characteristics
- Gate and Diffusion Capacitance
- Pass Transistors
- RC Delay Models

    
# Introduction

- So far, we have treated transistors as ideal switches
- An ON transistor passes a finite amount of current
  - Depends on terminal voltages
  - Derive current-voltage (I-V) relationships
- Transistor gate, source, drain all have capacitance
  - $I = C (\Delta V / \Delta t) \rightarrow \Delta t = (C / I) \Delta V$
  - Capacitance and current determine speed
- Also explore what a “degraded level” really means


 
# MOS Capacitor


- Gate and body form MOS capacitor
- Operating modes
  - Accumulation
  - Depletion
  - Inversion



Example with an NMOS capacitor

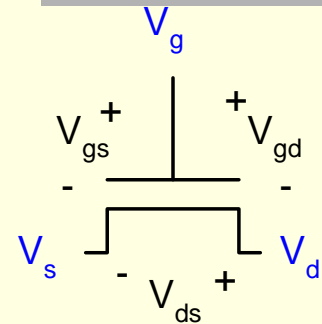
# Terminal Voltages

- Mode of operation depends on  $V_g$ ,  $V_d$ ,  $V_s$ 
  - $V_{gs} = V_g - V_s$
  - $V_{gd} = V_g - V_d$
  - $V_{ds} = V_d - V_s = V_{gs} - V_{gd}$
- Source and drain are symmetric diffusion terminals
  - However,  $V_{ds} \geq 0$
- NMOS body is grounded. First assume source may be grounded or may be at a voltage above ground.
- Three regions of operation
  - *Cutoff*
  - *Linear*
  - *Saturation*


 
# nMOS Cutoff

- Let us assume  $V_s = V_b$
- No channel, if  $V_{gs} = 0$
- $I_{ds} = 0$



# NMOS Linear


- Channel forms if  $V_{gs} > V_t$
- No Current if  $V_{ds} = 0$

- Linear Region:

- If  $V_{ds} > 0$ , Current flows from d to s ( $e^-$  from s to d)


- $I_{ds}$  increases linearly with  $V_{ds}$  if  $V_{ds} > V_{gs} - V_t$ .

- Similar to linear resistor

 
 
# NMOS Saturation

- Channel pinches off if  $V_{ds} > V_{gs} - V_t$ .
- $I_{ds}$  “independent” of  $V_{ds}$ , i.e., current saturates
- Similar to current source







# I-V Characteristics

---

- In Linear region,  $I_{ds}$  depends on
  - How much charge is in the channel
  - How fast is the charge moving

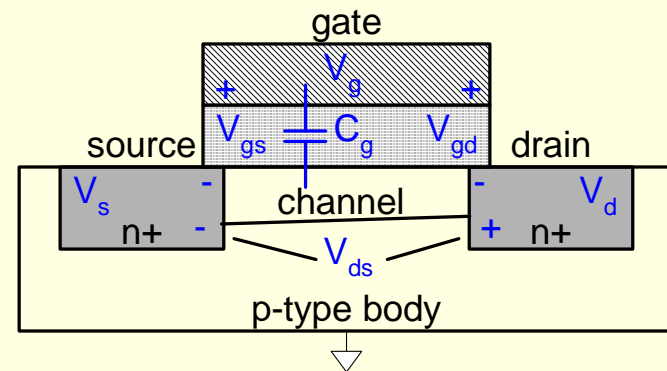
 
# Channel Charge

- MOS structure looks like parallel plate capacitor while operating in inversion
  - Gate – oxide (dielectric) – channel
- $Q_{\text{channel}} =$


  
# Channel Charge



- MOS structure looks like parallel plate capacitor while operating in inversion
  - Gate – oxide – channel
- $Q_{\text{channel}} = CV$
- $C =$


  
# Channel Charge

- MOS structure looks like parallel plate capacitor while operating in inversion
  - Gate – oxide – channel
- $Q_{\text{channel}} = CV$
- $C = C_g = \epsilon_{\text{ox}} WL/t_{\text{ox}} = C_{\text{ox}} WL$
- $V = V_{\text{gc}} - V_t = (V_{\text{gs}} - V_{\text{ds}}/2) - V_t$

$$C_{\text{ox}} = \epsilon_{\text{ox}} / t_{\text{ox}}$$



# Carrier velocity

- Charge is carried by e-
- Carrier velocity  $v$  proportional to lateral E-field between source and drain
- $v = \mu E$        $\mu$  called mobility
- $E = V_{ds}/L$
- Time for carrier to cross channel:
  - $t = L / v$

# NMOS Linear I-V

- Now we know

- How much charge  $Q_{\text{channel}}$  is in the channel
- How much time  $t$  each carrier takes to cross

$$I_{ds} = \frac{Q_{\text{channel}}}{t}$$

$$= \mu C_{\text{ox}} \frac{W}{L} \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$= \beta \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$\beta = \mu C_{\text{ox}} \frac{W}{L}$$

# NMOS Saturation I-V

- If  $V_{gd} < V_t$ , channel pinches off near drain
  - When  $V_{ds} > V_{dsat} = V_{gs} - V_t$
- Now drain voltage no longer increases current

$$\begin{aligned} I_{ds} &= \beta \left( V_{gs} - V_t - \frac{V_{dsat}}{2} \right) V_{dsat} \\ &= \frac{\beta}{2} (V_{gs} - V_t)^2 \end{aligned}$$

# NMOS I-V Summary


- Shockley 1<sup>st</sup> order transistor models (valid for Large channel devices only)

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$


 
# Example

- For a 0.6  $\mu\text{m}$  process ([MOSIS site](#))
  - From AMI Semiconductor
  - $t_{\text{ox}} = 100 \text{ \AA}$
  - $\mu = 350 \text{ cm}^2/\text{V}^*\text{s}$
  - $V_t = 0.7 \text{ V}$
- Plot  $I_{\text{ds}}$  vs.  $V_{\text{ds}}$ 
  - $V_{\text{gs}} = 0, 1, 2, 3, 4, 5$
  - Use  $W/L = 4/2 \lambda$



$$\beta = \mu C_{\text{ox}} \frac{W}{L} = (350) \left( \frac{3.9 \cdot 8.85 \cdot 10^{-14}}{100 \cdot 10^{-8}} \right) \left( \frac{W}{L} \right) = 120 \frac{W}{L} \mu\text{A}/\text{V}^2$$

# PMOS I-V

- All dopings and voltages are inverted for PMOS
- Mobility  $\mu_p$  is determined by holes
  - Typically 2-3x lower than that of electrons  $\mu_n$
  - 120 cm<sup>2</sup>/V\*s in AMI 0.6  $\mu\text{m}$  process
- Thus PMOS must be wider to provide same current
  - In this class, assume  $\mu_n / \mu_p = 2$


# Capacitance

---

- Any two conductors separated by an insulator have capacitance
- Gate to channel capacitor is very important
  - Creates channel charge necessary for operation
- Source and drain have capacitance to body
  - Across reverse-biased diodes
  - Called diffusion capacitance because it is associated with source/drain diffusion

 
# Gate Capacitance

- Approximate channel as connected to source
- $C_{gs} = \epsilon_{ox} WL/t_{ox} = C_{ox} WL = C_{permicron} W$
- $C_{permicron}$  is typically about 2 fF/ $\mu\text{m}$



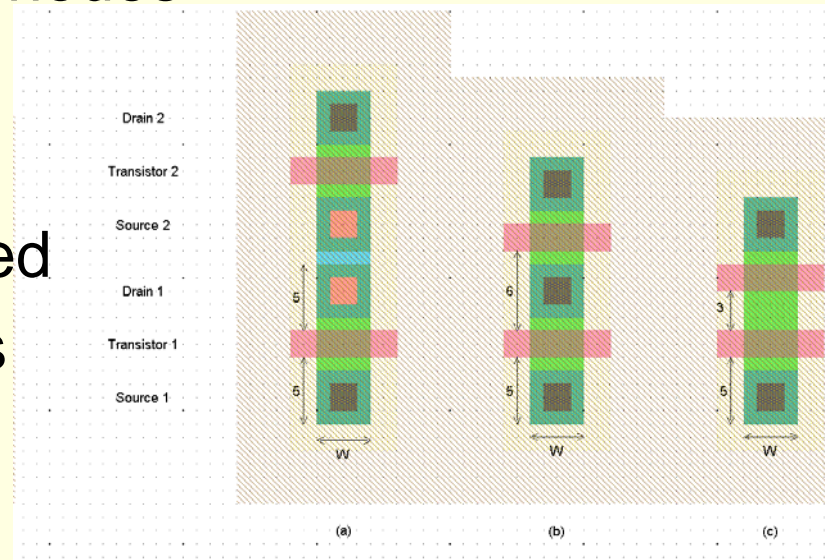
# Diffusion Capacitance

- $C_{sb}$ ,  $C_{db}$
- Undesirable, called *parasitic* capacitance
- Capacitance depends on area and perimeter
  - Use small diffusion nodes
  - Comparable to  $C_g$  for contacted diff
  - $\frac{1}{2} C_g$  for uncontacted
  - Varies with process



 
# Pass Transistors

- We have assumed source is grounded
- What if source  $> 0$ ?
  - e.g. pass transistor passing  $V_{DD}$






 
# NMOS Pass Transistors

- We have assumed source is grounded
- What if source  $> 0$ ?
  - e.g. pass transistor passing  $V_{DD}$
- Let  $V_g = V_{DD}$ 
  - Now if  $V_s > V_{DD} - V_t$ ,  $V_{gs} < V_t$
  - Hence transistor would turn itself off
- NMOS pass transistors **pull-up** no higher than  $V_{DD} - V_{tn}$ 
  - Called a degraded “1”
  - Approach degraded value slowly (low  $I_{ds}$ )
- PMOS pass transistors **pull-down** no lower than  $V_{tp}$ 
  - Called a degraded “0”







# Pass Transistor Ckts

    



# Pass Transistor Ckts

    


# Effective Resistance

- Shockley models have limited value
  - Not accurate enough for modern transistors
  - Too complicated for much hand analysis
- Simplification: treat transistor as resistor
  - Replace  $I_{ds}(V_{ds}, V_{gs})$  with effective resistance  $R$ 
    - $I_{ds} = V_{ds}/R$
  - $R$  averaged across switching of digital gate
- Too inaccurate to predict current at any given time
  - But good enough to predict RC delay
 
# RC Delay Model

- Use equivalent circuits for MOS transistors
  - Ideal switch + capacitance and ON resistance
  - Unit nMOS has resistance  $R$ , capacitance  $C$
  - Unit pMOS has resistance  $2R$ , capacitance  $C$
- Capacitance proportional to width
- Resistance inversely proportional to width




# RC Values

- Capacitance
  - $C = C_g = C_s = C_d = 2 \text{ fF}/\mu\text{m}$  of gate width
  - Values similar across many processes
- Resistance
  - $R \approx 6 \text{ K}\Omega \cdot \mu\text{m}$  in  $0.6\mu\text{m}$  process
  - Improves with shorter channel lengths
- Unit transistors
  - May refer to minimum contacted device ( $4/2 \lambda$ )
  - Or maybe  $1 \mu\text{m}$  wide device
  - Doesn't matter as long as you are consistent

 
# Inverter Delay Estimate

- Estimate the delay of a fanout-of-1 inverter



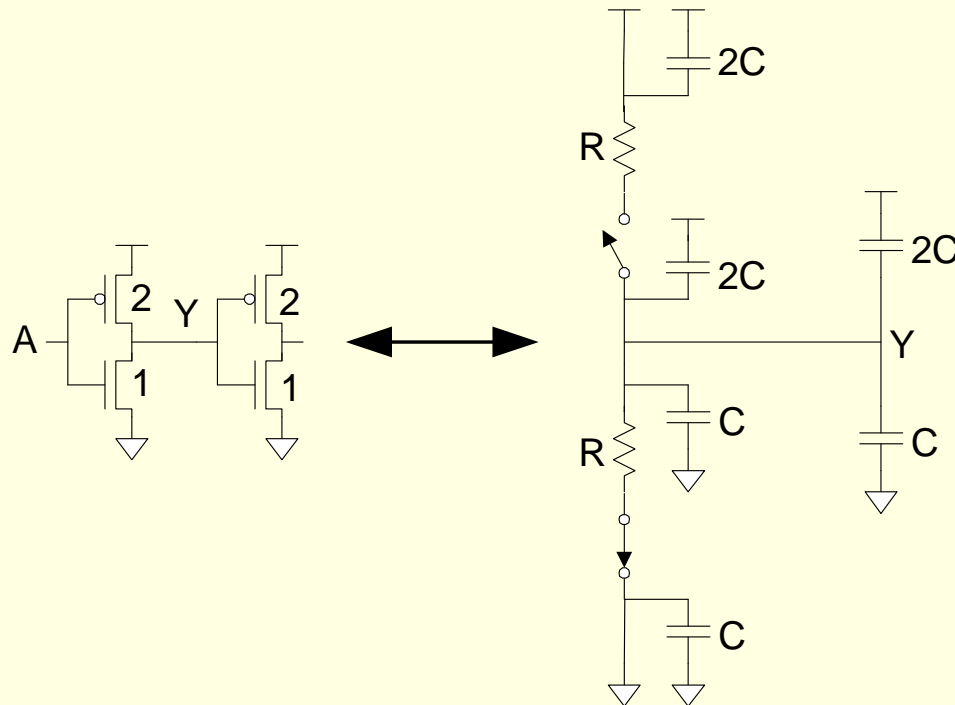
# Inverter Delay Estimate

- Estimate the delay of a fanout-of-1 inverter



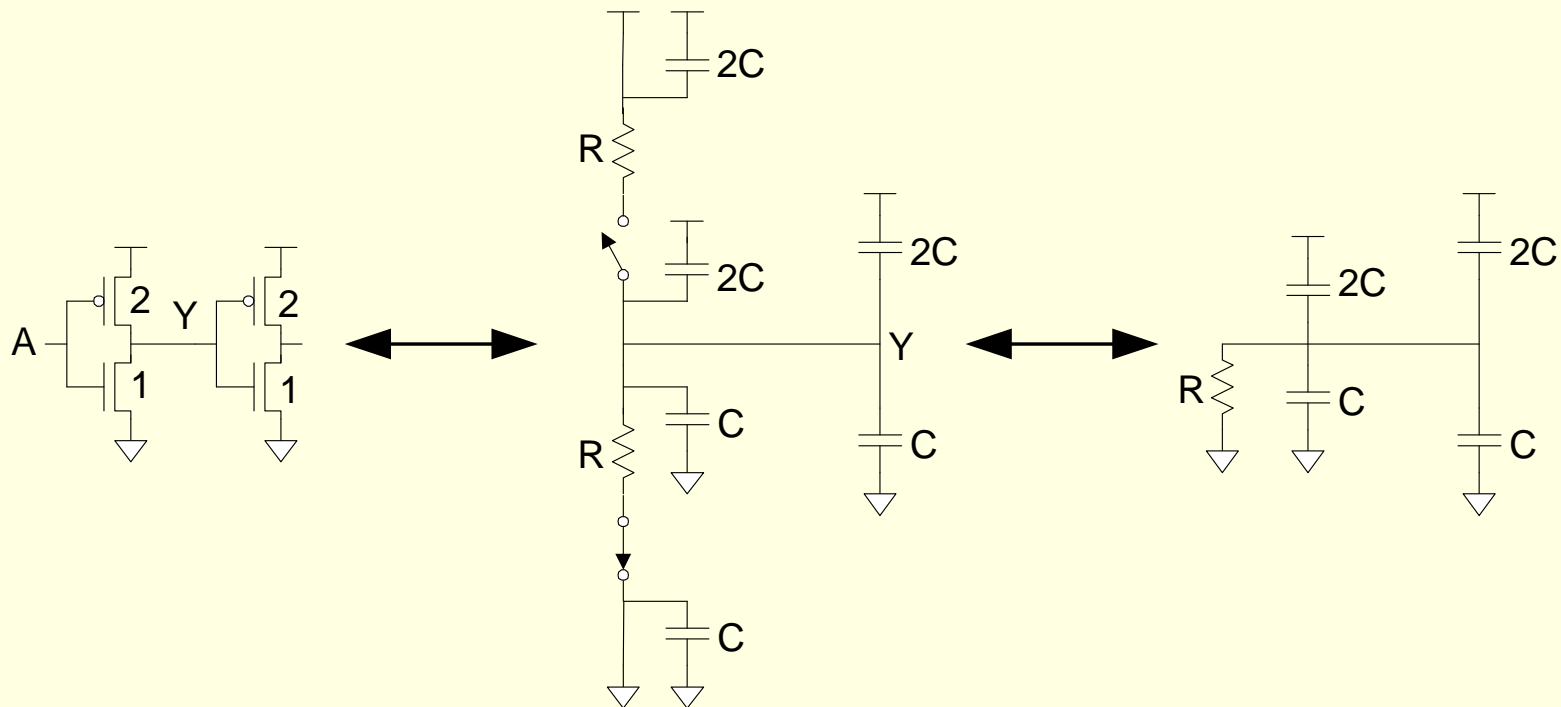
# Inverter Delay Estimate

- Estimate the delay of a fanout-of-1 inverter


 
# Inverter Delay Estimate

- Estimate the delay of a fanout-of-1 inverter



$$d = 6RC$$